

VLSI LAB 1 EE513

Experiment No. 09

Pawan Kumar
(214102412)

EEE department, Indian Institute of Technology Guwahati

13th november 2021

Design an HDL-based 32-bit processor (Instruction decode (Instruction decoder + controller) + Instruction execute (ALU)+register write (Register Bank)) which executes the following 10 instructions:

ADD SUB SLL SLT SLTU XOR SRL SRA OR AND

Objective:

Perform post-synthesis simulations for a basic 32-bit processor which executes the aforementioned instructions. The processor will basically have the following modules:

- A 32-bit register bank which will have 32 registers and each register can store 32-bit data.
- An instruction decoder module which will slice the 32-bit instructions into the corresponding fields opcode, function and rs1, rs2 and rd values.
- A controller module which will generate a corresponding signal for the respective operations depending function and opcode.
- 32-bit ALU for processing the data present in rs1 and rs2 registers.
- Register write to store the result back into rd register in the register bank.

Tool Used:


Xilinx 2019.1

Theory:

32 bit processor can process 32 bit Instructions per clock cycle. It operates the given function (In our case the functions are mentioned in above page) between two 32 bit data (which is called operands) and provides result of 32 bit too.

In more technical terms, this means processors can work with 32-bit binary numbers (decimal number up to 4,294,967,295). Anything larger and the computer would need to break the data into smaller pieces.

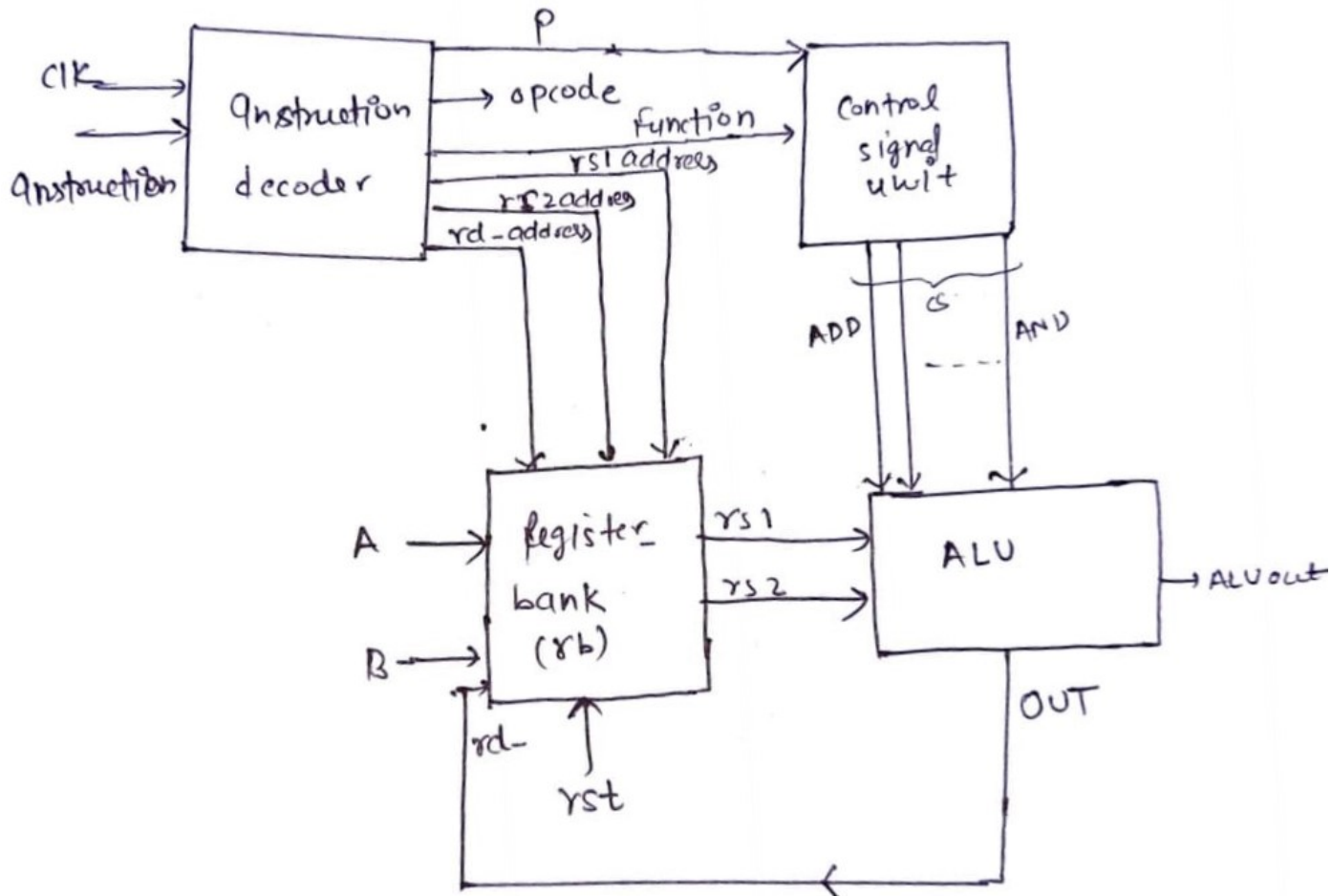Each instruction have opcode of 7 bit(0 to 6),function of 3 bit(12 to 14),address of 1st and 2nd operands (rs1 (bit 15-19), rs2 (bit 20-24)) and Address of result also of 5 bit (rd (bit 7-11)). 31th bit of instruction for differentiate between ADD and SUB, SRL and SRA.



Basic block diagram of 32 bit processor

Instruction Decoder:

When we provide the 32 bit instruction to processor this decoder decodes the 7-bit opcode, 5 bit address of Register (rs1,rs2 and rd) , 3 bit function.

- Opcode 7 bit (0-6)
- Register addresses (for rs1, rs2 and rd) of 5 bit
- Function 3 bit
- p is 1 bit (31th bit)

Register bank:

Basically register bank (32X32) is capable of storing 32 bit data at each location. The operands of 32 bit data is written at the address of operands(rs1 and rs2) and the result will be overwrite at the address of rd.

Control signal unit:

It will take the input as function and bit p and accordingly output will be the required function as (ADD SUB SLL SLT SLTU XOR SRL SRA OR AND).

- Out cs is of 4 bit which tells the operator.

ALU:

The main functionality of this unit is to performing the given operation between two 32 bit data and providing the result which will be stored in given address 32 bit register.

Instruction set Specification of the 32-bit processor:


31	25	24	20	19	15	14 func	12	11	7	6 opcode	0	
0000000		rs2		rs1		000		rd		0110011		ADD
0100000		rs2		rs1		000		rd		0110011		SUB
0000000		rs2		rs1		001		rd		0110011		SLL
0000000		rs2		rs1		010		rd		0110011		SLT
0000000		rs2		rs1		011		rd		0110011		SLTU
0000000		rs2		rs1		100		rd		0110011		XOR
0000000		rs2		rs1		101		rd		0110011		SRL
0100000		rs2		rs1		101		rd		0110011		SRA
0000000		rs2		rs1		110		rd		0110011		OR
0000000		rs2		rs1		111		rd		0110011		AND

Operations performed by ALU for each instruction:

S. No.	Operation	Functionality	Values to be taken for each operation to check the functionality
1	ADD	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] + \text{reg}[\text{rs2}]$	$\text{reg}[\text{rs1}] = 0000000F, \text{reg}[\text{rs2}] = 0000000C$
2	SUB	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] - \text{reg}[\text{rs2}]$	$\text{reg}[\text{rs1}] = 0000000F, \text{reg}[\text{rs2}] = 0000000C$
3	SLL	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] \ll \text{lower 5 bits of reg}[\text{rs2}]$ (shift left logical)	$\text{reg}[\text{rs1}] = FF0000FF, \text{reg}[\text{rs2}] = 00000004$
4	SLT	$\text{reg}[\text{rd}] = 1, \text{ if } (\text{reg}[\text{rs1}] < \text{reg}[\text{rs2}])$ Set less than signed	$\text{reg}[\text{rs1}] = 70000000, \text{reg}[\text{rs2}] = F0000000$
5	SLTU	$\text{reg}[\text{rd}] = 1, \text{ if } (\text{reg}[\text{rs1}] < \text{reg}[\text{rs2}])$ Set less than unsigned	$\text{reg}[\text{rs1}] = 70000000, \text{reg}[\text{rs2}] = F0000000$
6	XOR	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] \wedge \text{reg}[\text{rs2}]$	$\text{reg}[\text{rs1}] = 0000000F, \text{reg}[\text{rs2}] = 0000000C$
7	SRL	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] \gg \text{lower 5 bits of reg}[\text{rs2}]$ (shift right logical)	$\text{reg}[\text{rs1}] = FF0000FF, \text{reg}[\text{rs2}] = 00000004$
8	SRA	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] \ggg \text{lower 5 bits of reg}[\text{rs2}]$ (shift right arithmetic)	$\text{reg}[\text{rs1}] = FF0000FF, \text{reg}[\text{rs2}] = 00000004$
9	OR	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] \mid \text{reg}[\text{rs2}]$	$\text{reg}[\text{rs1}] = 0000000F, \text{reg}[\text{rs2}] = 0000000C$
10	AND	$\text{reg}[\text{rd}] = \text{reg}[\text{rs1}] \& \text{reg}[\text{rs2}]$	$\text{reg}[\text{rs1}] = 0000000F, \text{reg}[\text{rs2}] = 0000000C$

Observations:

Schematic of the processor:

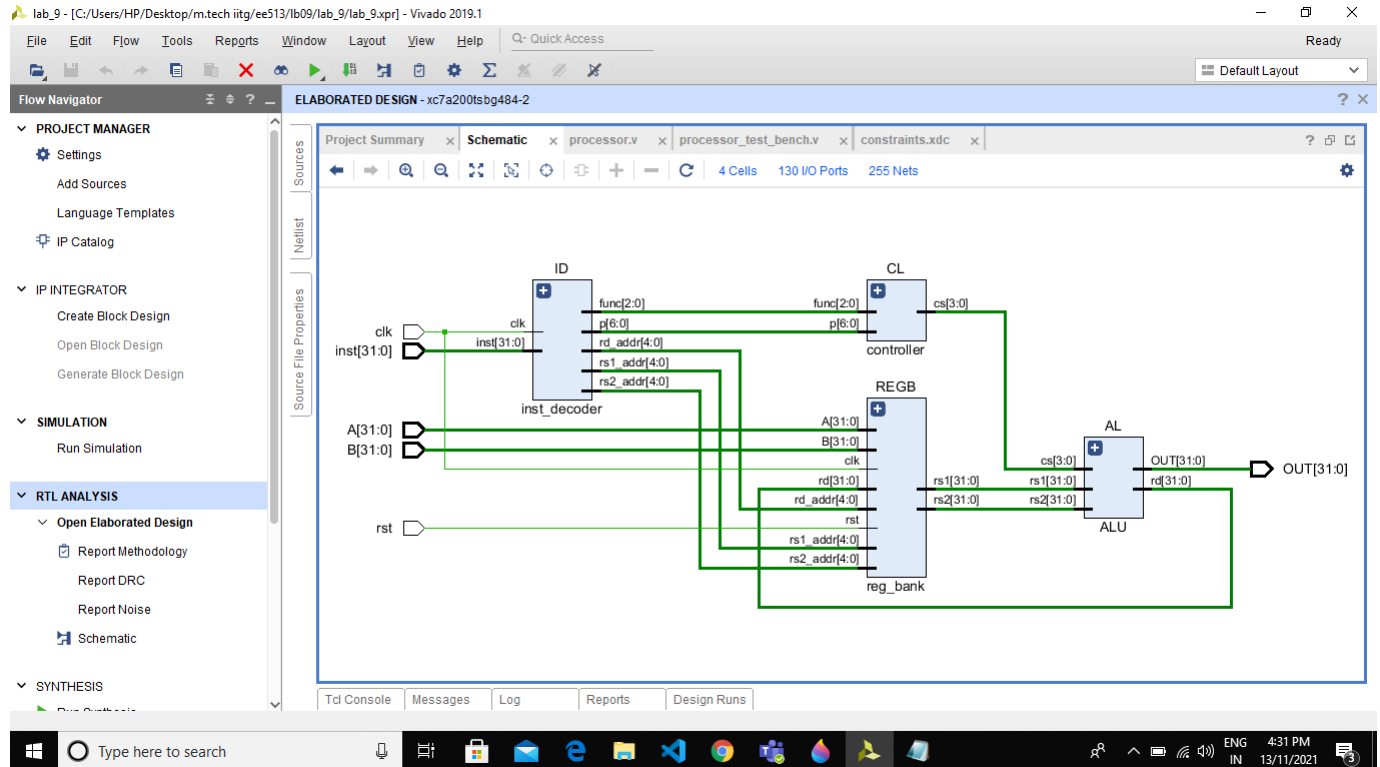


No of LUTs and Flip Flops used in the processor:


Design Runs																		
Progress	Incremental	WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	LUT	FF	BRAMs	URAM	DSP	LUTRAM	Start	Elapsed	Run Strategy
100%	Off									2617	1088	0.0	0	0	0	11/13/21, 4:34 PM	00:04:06	Vivado Synthesis Defaults (Vivado Synthe
100%	Off	3.680	0.000	0.338	0.000		0.000	0.190	0	2617	1088	0.0	0	0	0	11/13/21, 4:39 PM	00:07:48	Vivado Implementation Defaults (Vivado I

Output Wave form of the processor:


SLL,5 bit left shift:

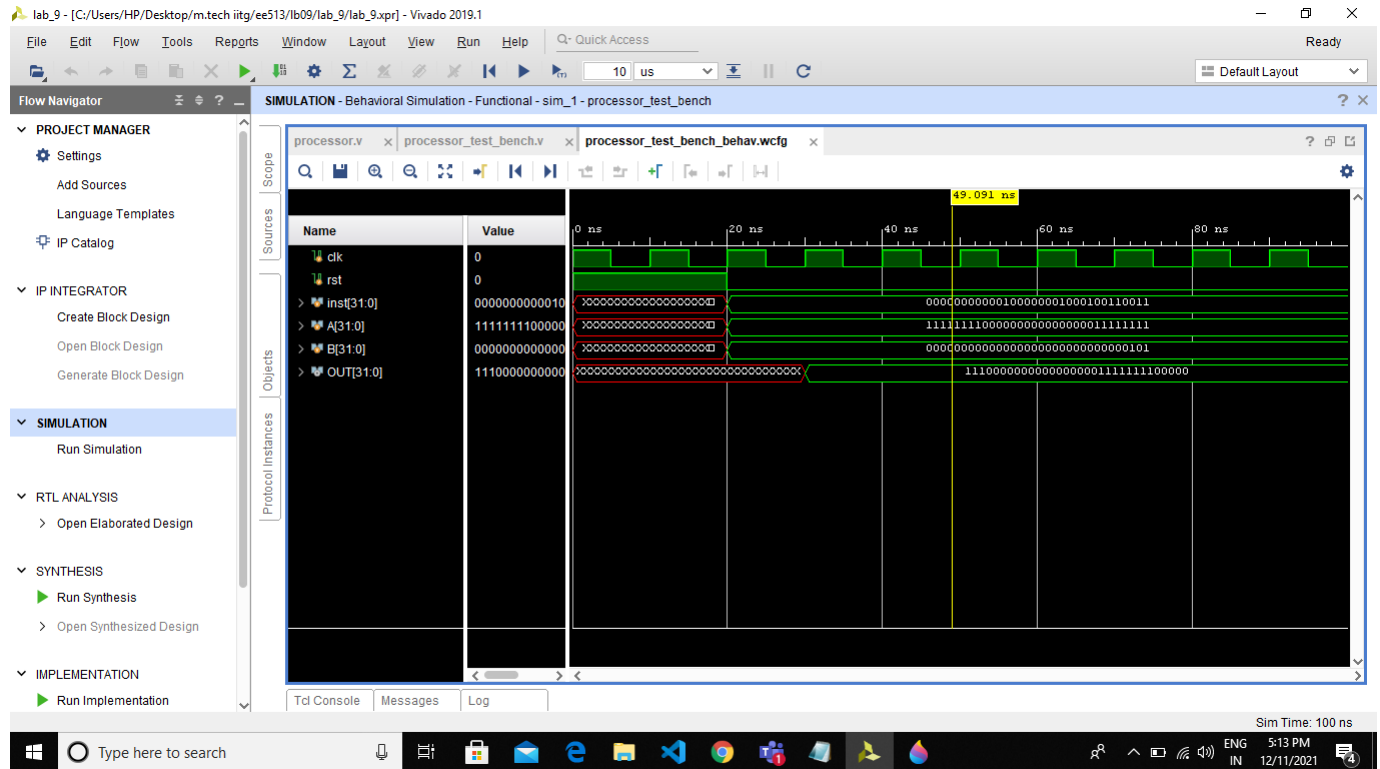

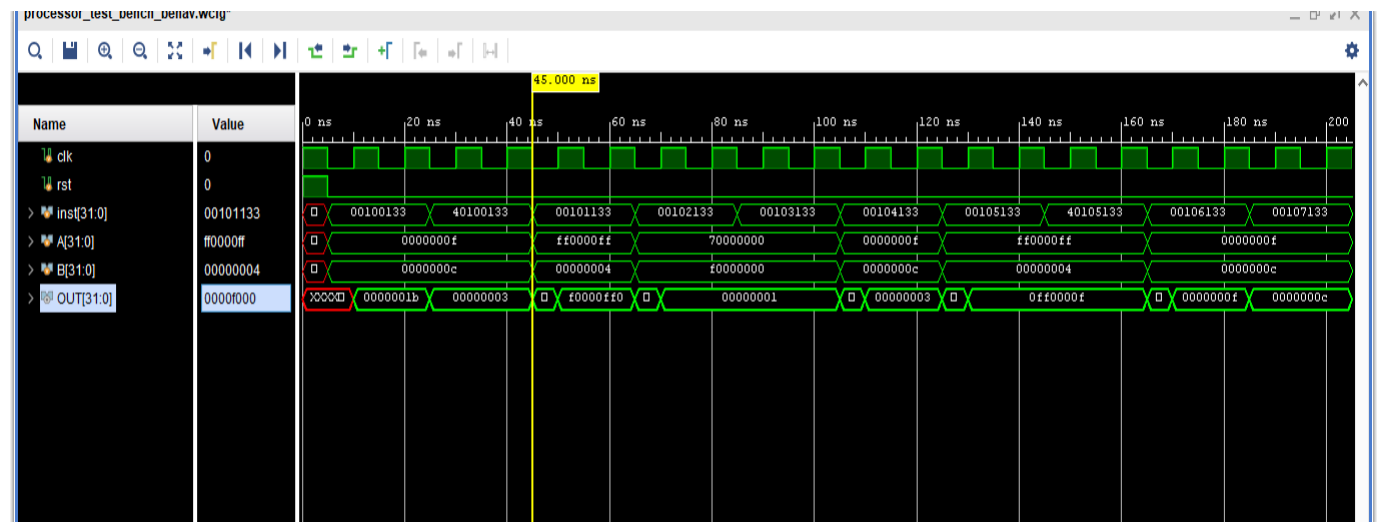
waveform for all the function given in the table earlier:



Delay Analysis:

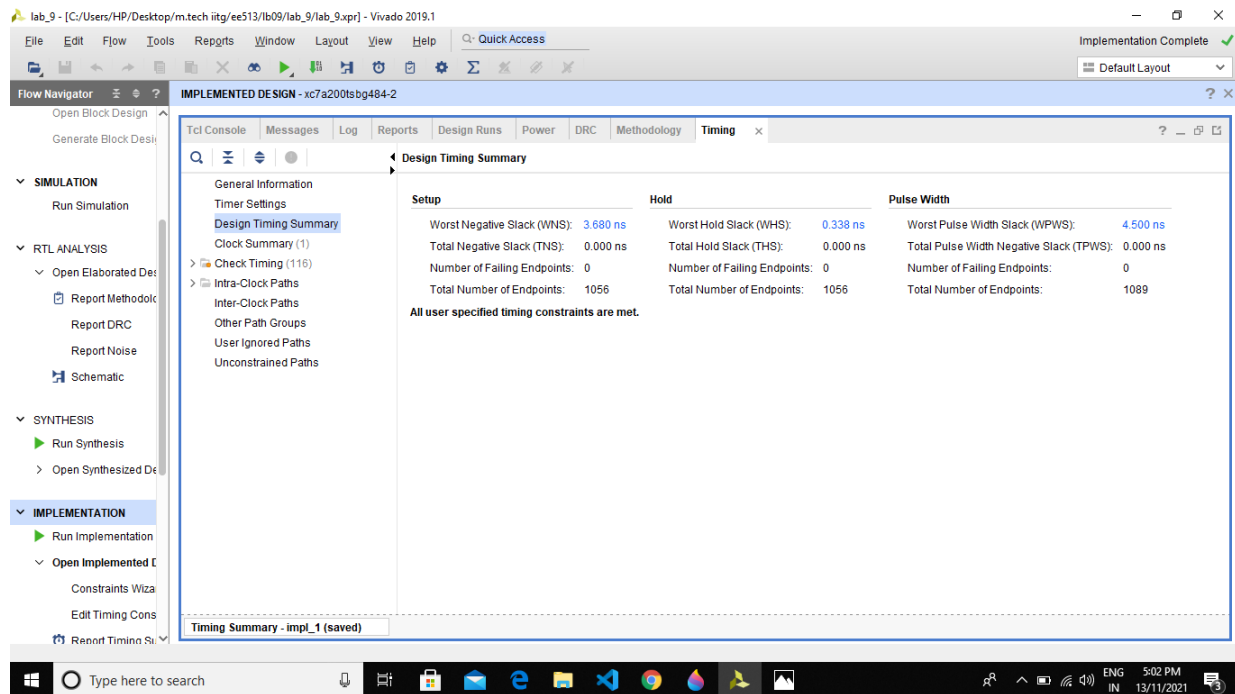

Power Analysis:

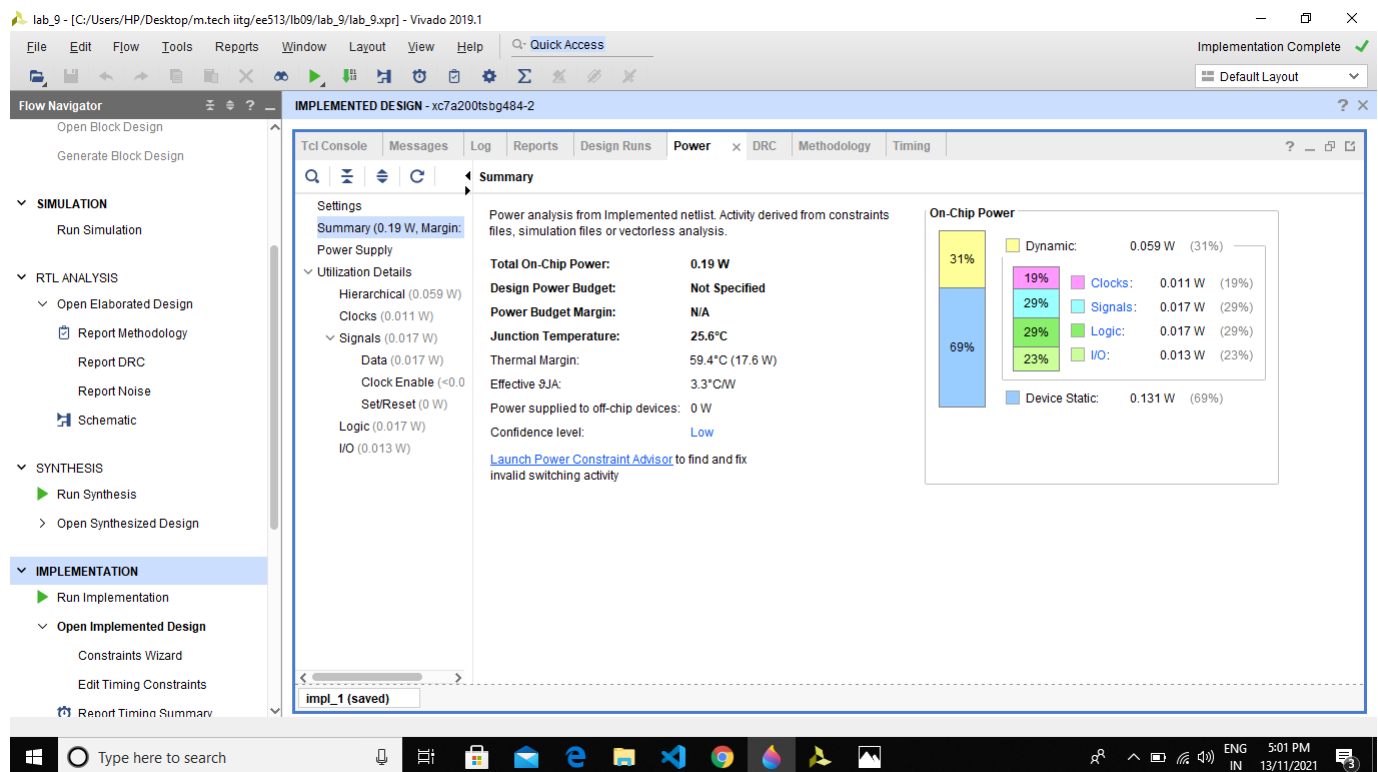

Result:

	No. of LUTs	No. of Flip Flops	Power	Delay
Processor	2617	1088	0.19 W	3.680 ns

Conclusion:

- I have successfully designed and implemented the 32 bit processor which will perform the given 32 bit instruction.
- I have taken a basic instruction in test bench for shifting left of 32 bit data. rs1 will be shift as much as the lower 5 bit of rs2. In this case lower bit of rs2 is 01101, It means rs1 32 bit data will shift 5 bit left and we can see in the waveform of SLL.
- I have also performed all the instruction given in the table and output wave form is uploaded in above page.
- No of LUTs and Flip Flops used are 2617 and 1088 respectively.
- Required power is 0.19 W and delay is 3.68 ns.